

ELEC-2210

Digital Electronics

FROM: Jacob Howard

TO: Jonathan

DATE: 9/29/20

LAB SECTION: 002 (Tuesday, 1:00pm-2:50 pm)

EXPERIMENT 7:

BJT Transistors

Introduction

In this lab, we learned the function of BJT Transistors. This was our first Lab with BJT transistors, so we learned how they work and control output current. This lab had 5 steps, although, we did not have to do the last step.

Step 1

In Step 1, we were asked to measure the forced I_B output of the NPN transistor. Measuring the transistor was quite simple. The graph is shown in *Figure 1*. Also the graph data is shown below in *Data 1*.

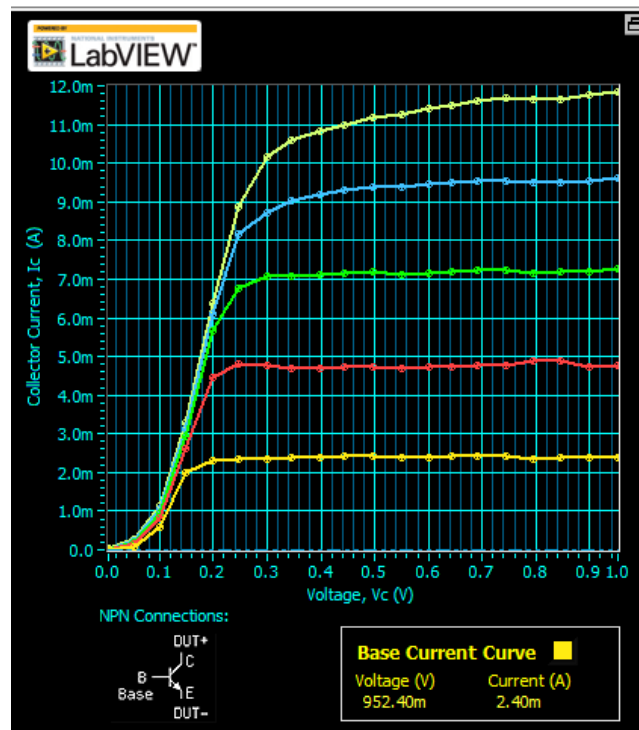


Figure 1

9/29/2020 1:22 PM

Base current (μA): 15.0

Collector Voltage (V),Collector Current (A)

0.00432970 0.00000518

0.05252076 0.00007091

0.09948961 0.00033757

0.14763079 0.00083867

0.20031521 0.00148060

0.24692075 0.00203975

Base current (μA): 30.0

Collector Voltage (V),Collector Current (A)

0.00432970 0.00000835

0.05252076 0.00011862

0.09948961 0.00045369

0.14763079 0.00101358

0.20031521 0.00172977

0.24692075 0.00240364

Base current (μA): 45.0

Collector Voltage (V),Collector Current (A)

0.00432970 0.00001200

0.05252076 0.00015761

0.09948961 0.00053347

0.14763079 0.00112765

0.20031521 0.00184949

0.24692075 0.00256690

Base current (μA): 60.0

Collector Voltage (V),Collector Current (A)

0.00432970 0.00001551

0.05252076 0.00019240

0.09948961 0.00059455

0.14763079 0.00120119

0.20031521 0.00194470


0.24692075 0.00269291

Base current (μA): 75.0	
Collector Voltage (V), Collector Current (A)	
0.00432970	0.00002052
0.05252076	0.00021786
0.09948961	0.00064391
0.14763079	0.00125636
0.20031521	0.00200417
0.24692075	0.00282494

Data 1

Step 2

For part 2, we connected the circuit that was given to us in *Figure 2*. Our goal was to measure how I_C changes with V_{CE} for forced base-emitter voltages. We were provided a LabView program to download and use to get the graph and data. The graph is shown in *Figure 3* and the data for the graph is shown in *Table 1*.

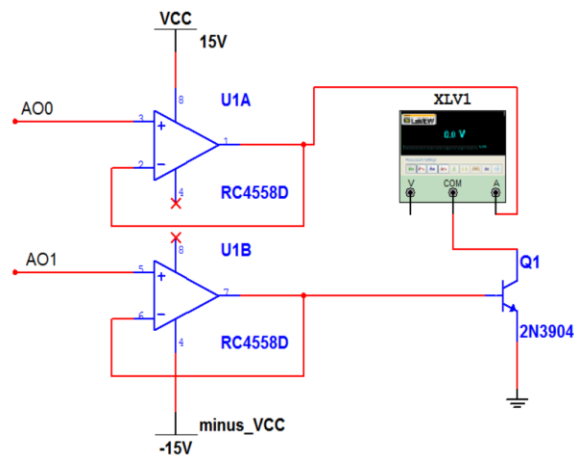*Figure 1*

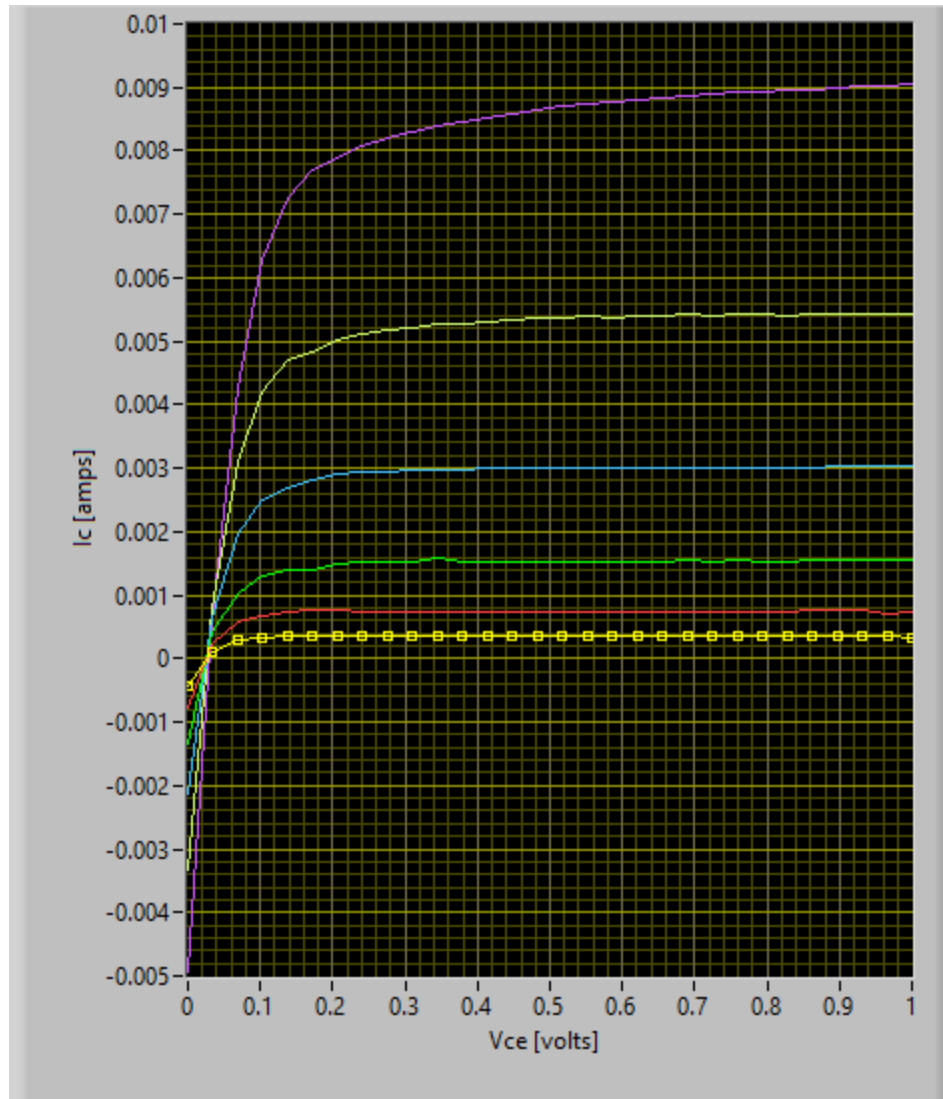



Figure 2

Vce [volts] - Plot 0	Ic [amps] - Plot 0	Vce [volts] - Plot 1	Ic [amps] - Plot 1	Vce [volts] - Plot 2	Ic [amps] - Plot 2	Vce [volts] - Plot 3	Ic [amps] - Plot 3	Vce [volts] - Plot 4	Ic [amps] - Plot 4	Vce [volts] - Plot 5	Ic [amps] - Plot 5
0	-0.000418436	0	-0.000766973	0	-0.00133335	0	-0.00212402	0	-0.00333116	0	-0.00494758
0.0344828	0.000109724	0.0344828	0.000216611	0.0344828	0.000411556	0.0344828	0.00062773	0.0344828	0.000809937	0.0344828	0.000646744
0.0689655	0.0002827	0.0689655	0.000567548	0.0689655	0.00103202	0.0689655	0.00195837	0.0689655	0.0031129	0.0689655	0.00427667
0.103448	0.000336974	0.103448	0.000677205	0.103448	0.00130837	0.103448	0.00251183	0.103448	0.00421482	0.103448	0.00627356
0.137931	0.000361527	0.137931	0.000742186	0.137931	0.00138443	0.137931	0.00267742	0.137931	0.00470551	0.137931	0.00724625
0.172414	0.000354512	0.172414	0.000760278	0.172414	0.00140585	0.172414	0.0028168	0.172414	0.00484673	0.172414	0.00770056
0.206897	0.000344728	0.206897	0.000755478	0.206897	0.00148929	0.206897	0.00289525	0.206897	0.00501158	0.206897	0.00787576
0.241379	0.000346574	0.241379	0.00074754	0.241379	0.00151107	0.241379	0.00293144	0.241379	0.0051133	0.241379	0.00807901
0.275862	0.000347312	0.275862	0.000743294	0.275862	0.00152492	0.275862	0.00294584	0.275862	0.00517755	0.275862	0.00820768
0.310345	0.000341959	0.310345	0.000741632	0.310345	0.00152436	0.310345	0.0029702	0.310345	0.00522241	0.310345	0.0083022
0.344828	0.000343066	0.344828	0.00073794	0.344828	0.0015827	0.344828	0.00297814	0.344828	0.00526136	0.344828	0.00838804
0.37931	0.000346389	0.37931	0.000732587	0.37931	0.00152695	0.37931	0.00298423	0.37931	0.0052848	0.37931	0.00846004
0.413793	0.000344174	0.413793	0.000746247	0.413793	0.00152436	0.413793	0.00299162	0.413793	0.00531877	0.413793	0.00852373
0.448276	0.000349528	0.448276	0.000739786	0.448276	0.00152898	0.448276	0.00299845	0.448276	0.00534332	0.448276	0.0085852
0.482759	0.00034159	0.482759	0.000740155	0.482759	0.00153212	0.482759	0.00300325	0.482759	0.00536012	0.482759	0.00864243
0.517241	0.000342513	0.517241	0.000743109	0.517241	0.00153156	0.517241	0.00299863	0.517241	0.00535809	0.517241	0.00869892
0.551724	0.00034159	0.551724	0.000744771	0.551724	0.00153175	0.551724	0.00300048	0.551724	0.00538652	0.551724	0.00874359
0.586207	0.000345651	0.586207	0.000744032	0.586207	0.00152658	0.586207	0.00300989	0.586207	0.00538338	0.586207	0.00878199
0.62069	0.000341774	0.62069	0.000749755	0.62069	0.00152806	0.62069	0.00301396	0.62069	0.00539834	0.62069	0.00881448
0.655172	0.000347866	0.655172	0.000741817	0.655172	0.00153563	0.655172	0.00301322	0.655172	0.00540406	0.655172	0.00884457
0.689655	0.000345651	0.689655	0.000744586	0.689655	0.00153987	0.689655	0.00300989	0.689655	0.00541993	0.689655	0.00887485
0.724138	0.000342328	0.724138	0.000744032	0.724138	0.00153655	0.724138	0.00301322	0.724138	0.00541384	0.724138	0.00889349
0.758621	0.000345097	0.758621	0.000743478	0.758621	0.00154061	0.758621	0.00301857	0.758621	0.00542086	0.758621	0.00891472
0.793103	0.000343989	0.793103	0.000745324	0.793103	0.00153766	0.793103	0.00301968	0.793103	0.00543452	0.793103	0.00893189
0.827586	0.000344105	0.827586	0.000743109	0.827586	0.00153581	0.827586	0.00301728	0.827586	0.00541403	0.827586	0.00895349
0.862069	0.000343251	0.862069	0.000756032	0.862069	0.00154264	0.862069	0.00301672	0.862069	0.00541809	0.862069	0.00896913
0.896552	0.000344174	0.896552	0.000758247	0.896552	0.00154338	0.896552	0.00302429	0.896552	0.00541661	0.896552	0.00899263
0.931034	0.000342882	0.931034	0.000758431	0.931034	0.00154947	0.931034	0.00302097	0.931034	0.00541883	0.931034	0.00901072
0.965517	0.000343066	0.965517	0.000704711	0.965517	0.00154596	0.965517	0.0030278	0.965517	0.00541661	0.965517	0.00902475
1	0.00039559	1	0.000747909	1	0.00154264	1	0.00302614	1	0.00542196	1	0.00904524

*Table 1**Table 2*

Step 3

In step 3, we were asked construct the circuit shown inn Figure 4. The circuit we constructed was essentially a BJT inverter, which could be used as an amplifier when bias point is set to the region where the output voltage changes fastest with the input voltage. We were provided another LabView program to provide 3 different graphs. The graphs are shown in *Figures 5 – 7*. The output starts to drop around $V_{in} = 1V$.

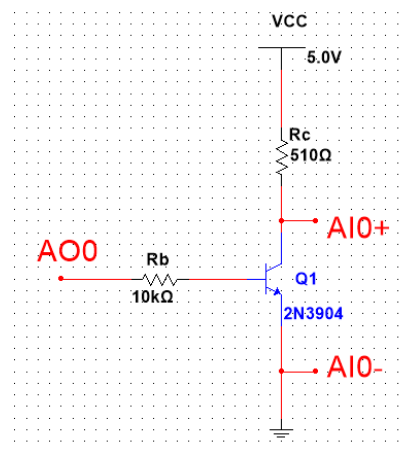*Figure 4*

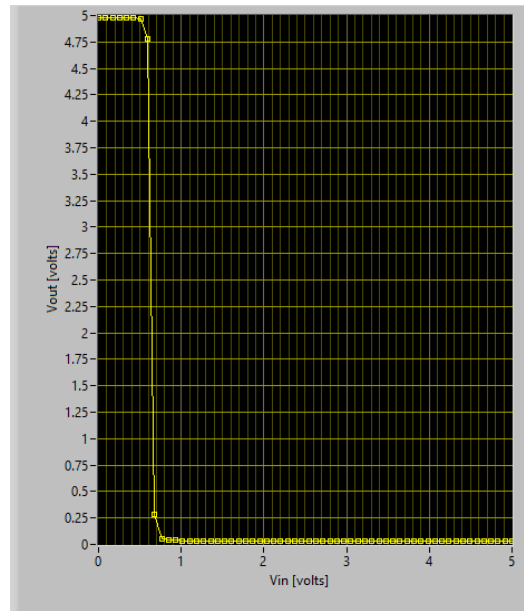


Figure 5


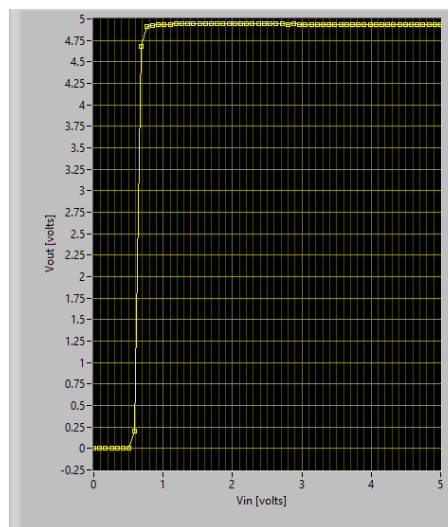
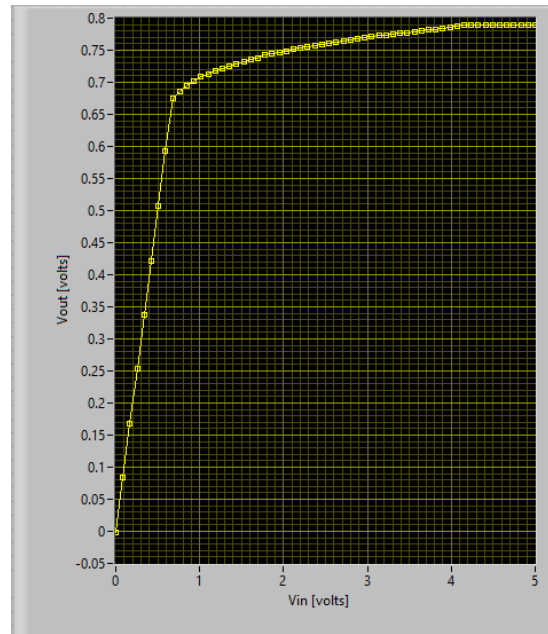


Figure 6

*Figure 7*

Step 4

In step 4, we were to demonstrate how the BJT really works. We were to consturc the circuit from Figure 8 onto the Breadboard. Having a low input voltage or current will turn the collector current off and a high input voltage or current turns the transistor on. This basically means the transistor can be used as a switch depending on what input voltage or current you provide. After demonstraiting to the TA how the BJT can function as a switch to turn off and on the LED, we were to record measurements. The measurements are provided below in *Table 2*.

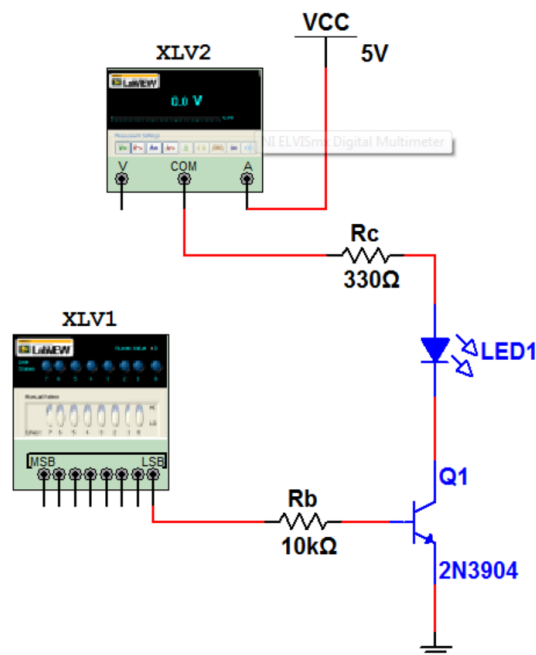

LED	On	Off
VCE	5V	0V
VBE	0.75V	0V
VBC	0.64V	3.47V
IB	0.415mA	0A
IC	8.57mA	0A

Conclusion

This was our first lab with BJT transistors. The lab was very interesting and helped us better understand how BJT Transistors worked. Overall, this lab was not too difficult and was very interesting , especially showing how we can use a transistor as a switch in a circuit.

