

PRACTICE TEST 1 ANSWER KEY

- 1.1 4.5
- 1.2 5.0
- 2 8.59
- 3.1 donors
- 3.2 answer is 1.1×10^{17} to compensate the background N_A and obtain desired n
- 3.3 0.1
- 4 The 1V side acts as source of electrons, Current flows from 5V to 1V
- 5.1 answer is 0.8V, the turn-on voltage of the junction given
- 5.2 1.3
- 5.3 see our Onenote "old test" in the test 1 section for a drawing. I_B is zero between 0 and 0.8V, the turn-on, then it increases linearly as $I_B = (V_{in} - V_{be})/R_b$
- 5.4 find I_c , then divide it by I_b , this is in saturation it turns out, 31.25
- 6.1 -4.5
- 6.2 The current is limited to mA range typical for LED operation
- 6.3 1.5
- 6.4 1.5
- 7.1 4.3
- 7.2 -10.7
- 7.3 -14.27
- 8.1 100
- 8.2 2.0
- 9 see our notes for a PNP design example. We also have this in the "old test 1" in Onenote.
- 10.1 $V_{in}=0V$, NMOS is off, PMOS must have same current, zero A, because PMOS $V_{gs} = -V_{dd}$, it is on, only possible V_{out} is V_{dd} , which makes $V_{DS}=0$ so that PMOS current is equal to Nmos current. Supply current is 0.
- 10.2 $V_{out}=0V$, currents are both 0. $V_{GS,pmos}=0V$, so PMOS is off. $V_{GS,nmos}=5V$, so NMOS is on, to have zero current, NMOS V_{DS} has to be zero, so $V_{out}=0V$.
- 10.3 for numerical example, see our "old test1" or our notes.

- 11.1** for intrinsic caps, when $V_{GS}=V_{DS}=V_{DD}$, transistor is in saturation, C_{gs} is $\frac{3}{2}C_{gc}$, C_{gd} is zero, so C_{gs} is larger than C_{gd} .
- 11.2** extrinsic C_{gs} and C_{gd} are proportional to width, extrinsic C_{gb} is proportional to length. See picture drawings in our notes for understanding why.
- 11.3** see the drawing in our notes, at zero V_{ds} , C_{gs} is equal to half of $\frac{1}{2} * C_{ox}'' * W * L$.