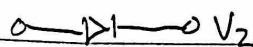



Prelab & Quiz Digitron



• if $V_1 > V_2$


D = Forward Bias

acts as Battery Source

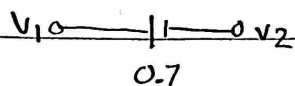


• If $V_1 < V_2$ D = Reverse Bias


acts as open circuit

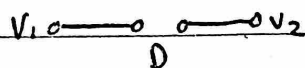


a)

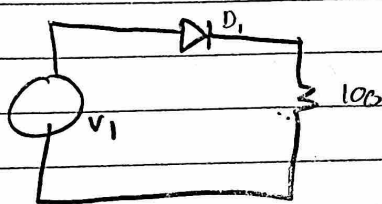

• if $V_1 = 5V$

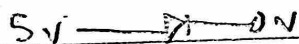


D = Forward Bias

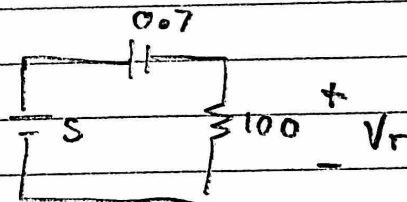


$$S = V_D + V_r$$

$$V_r = 5 - 0.7 = 4.3V$$

if $V_1 = -5V$

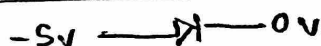

D = Reverse Bias

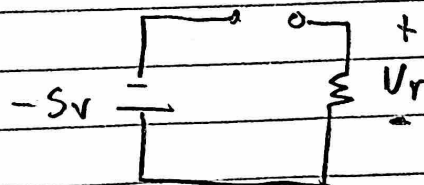


$$V_r = 0V$$

Lab Quiz 6 Digitron

20

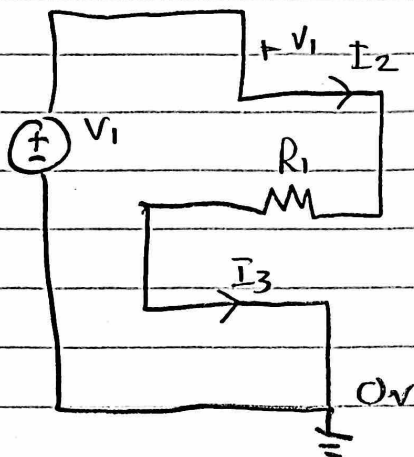assume, $b_2 + D_3$ in forward bias
 D_1, D_4 Reverse Bias



If $V_1 = +V_e$ then $I_1 = I_3 = \text{positive}$ ✓

$D_1, D_4 = \text{Reverse bias (So off)}$

$D_2, D_3 = \text{Forward bias (So ON)}$