

# Gradescope Practice Test

1)  $n = 3$   
 $V_{FS} = 8$   
 $V_{in} = 5.4V$   
 $V_{in} < V_{out}$

$$V_{lsb} = \frac{8}{2^3} = 1$$

$$\frac{V_{in}}{V_{lsb}} = 5.4 \rightarrow 5V$$

$$Range = V_{out} \pm \frac{1}{2} V_{lsb}$$

$$= 4.5 - 5.5 \text{ but } V_{in} < V_{out} \text{ so}$$

$$Range = 4.5 - 5$$

2) 10 binary GB

10 GBPS

time = ?

$$10 \text{ binary GB} = 10 \cdot \frac{2^{30} \text{ byte}}{\text{GB}} \cdot \frac{8 \text{ bits}}{\text{byte}} = 8.59 \times 10^{10} \text{ bits}$$

$$8.59 \times 10^{10} = 85.9 \text{ Gb}$$

$$time = \frac{85.9 \text{ Gbits}}{10 \text{ GBPS}} = 8.59 \text{ seconds}$$

3) a)  $\boxed{\text{don't}}$

b)  $L = 20 \text{ nm}$   
 $N_A = 10^{16}$   
 $n_i = 10^{10}$   
 $V_{sat} = 10^7$   
 $m_s = 200$

$$\text{target } n = 10^{17}$$

$$pn = n_i^2 \rightarrow p = \frac{n_i^2}{n} = 1000$$

$$p + N_d = n + N_A \rightarrow N_d = (n + N_A) - p$$

$$= 1.1e^{17}$$

c)  $V_{sat} = mE = n \cdot \frac{V}{L} = \frac{n \cdot V}{L}$   $\leftarrow \text{convert nm to cm}$


$$N = \frac{L \cdot V_{sat}}{m} = \frac{(20 \times 10^{-7}) \cdot 10^7}{200} = 0.1V$$

4) The two contacts of a n-type semiconductor are biased at 1V and 5V.

- The 1V side acts as the source of electrons.
- Current flows from 5V to 1V

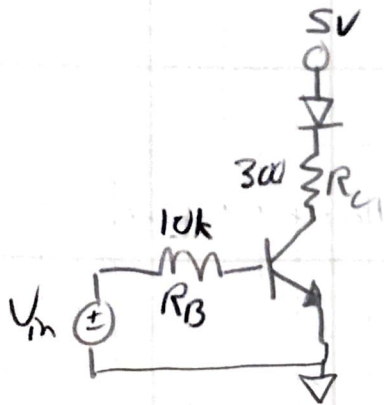5) NPN Switch

$$\beta_F = 200, V_{BE,on} = 0.8V, V_{CE,sat} = 0.2V, \text{Diode turn on} = 1.8V$$



a) At what  $V_{in}$  does the BE junction turn on?

$$V_{BE,on} = 0.8V \text{ so } V_{in} \text{ must equal } \boxed{0.8V}$$

b) At what  $V_{in}$  does the transistor enter Saturation?


$$V_{in} = V_{BE,on} + \frac{(5V - V_{CE,sat} - V_{diode,on})}{R_C} \times \frac{1}{\beta_F} \times R_B$$

$$V_{in} = 0.8 + \frac{(5 - 0.2 - 1.8)}{300} \times \frac{1}{200} \times 10,000 = \boxed{1.3V}$$


c)  $V_{in}$  sweeps from 0V to 5V, sketch  $I_B$

$$I_B = \frac{V_{in} - V_{BE,on}}{10k}$$

$$V_{BE,on} = 0.8V$$

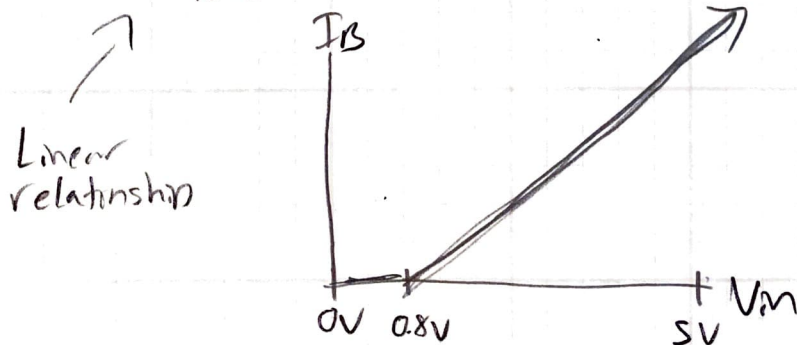


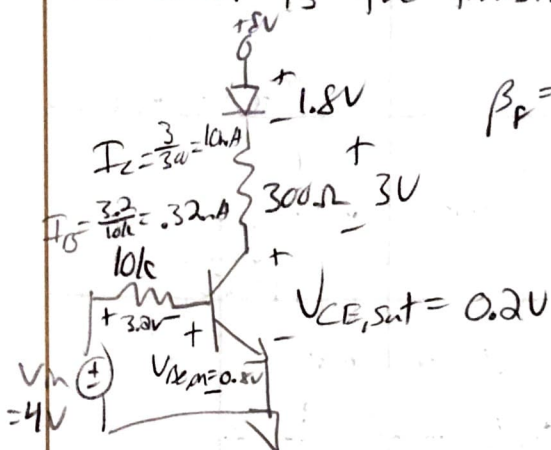d) What is the transistor current gain at  $V_{in} = 4V$ ?



$$\beta_F = \frac{I_C}{I_B} = \frac{10mA}{0.33mA} = 31.25$$

e)

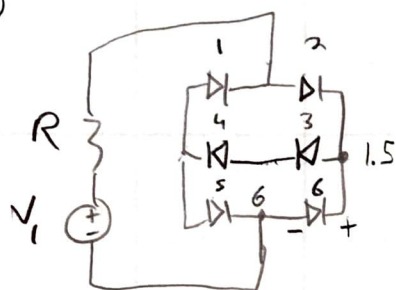

a) Find forward voltage across D6 for  $V_i = 15V$

$$1.5 - 6 = -4.5V$$

b) Why is  $R$  a few hundred  $\Omega$  instead of a few  $\Omega$ ?

A: Limit current to a mA range typical for LEDs

c) Forward Voltage of D4 when  $V_i = 15V$


$$+1.5V$$

d) Forward Voltage of D3 when  $V_i = -15V$

$$+1.5V$$



7)

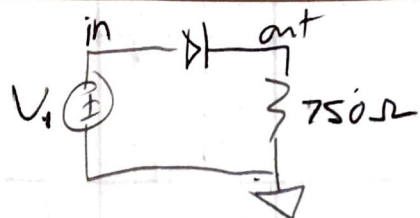

Turn-on = 0.7 V  
Switching from 5V to -10V

a)  $V_{out}$  before switching

$$V_{in} - V_{on} = 5 - 0.7 = \boxed{4.3 \text{ V}}$$

b)  $V_{out}$  after switching

$$V_{in} - V_{on} = -10 - 0.7 = \boxed{-10.7 \text{ V}}$$

c) Diode current after switching


$$I = \frac{V}{R} = \frac{-10.7}{750} = \boxed{-14.26 \text{ mA}}$$

8)

$$a) \beta_F = \frac{I_C}{I_B} = \boxed{100}$$

$$b) \beta_R = \frac{I_C}{I_B} = \boxed{2}$$

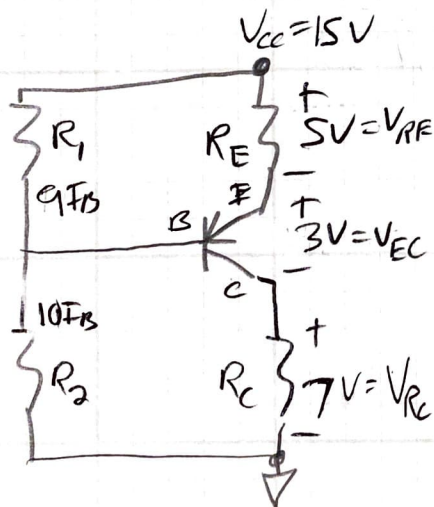a) Design a 4-resistor PNP circuit to achieve:  
 $V_{EC} = 3 \text{ V}$ ,  $I_C = 5 \text{ mA}$ ,  $\beta_F = 100$ ,  $V_{CC} = 15 \text{ V}$ ,  $\phi_E = 0.0258$ ,  $I_S = 10^{-15}$   
 Make feedback resistor drop 5V.



$$R_C = \frac{V_{RC}}{I_C} = \boxed{1.4 \text{ k}\Omega}$$

$$I_B = \frac{I_C}{\beta_F} = \frac{5 \text{ mA}}{100} = 50 \mu\text{A}$$

$$I_E = I_B + I_C = 50 \mu\text{A} + 5 \text{ mA} = 5.05 \text{ mA}$$

$$R_E = \frac{V_{RE}}{I_E} = \frac{5 \text{ V}}{5.05 \text{ mA}} = \boxed{990 \Omega}$$


$$V_{EB} = \phi_E \ln\left(\frac{I_E}{I_S}\right) = 0.0258 \ln\left(\frac{5 \text{ mA}}{10^{-15}}\right) = 0.75 \text{ V}$$

$$V_B = V_{CC} - V_{RE} - V_{EB} = 15 - 5 - 0.75 = 9.25 \text{ V}$$

$$R_2 = \frac{V_B}{10I_B} = \boxed{18.49 \text{ k}\Omega}$$

$$R_1 = \frac{V_B}{9I_B} = \boxed{12.78 \text{ k}\Omega}$$

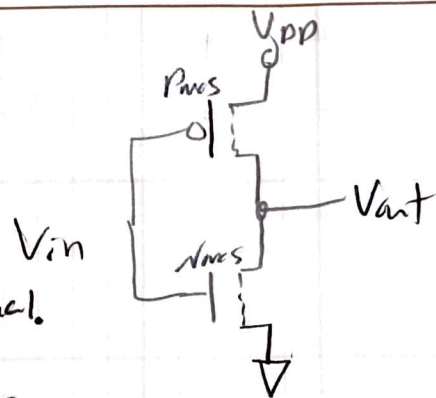- 10) NMOS =  $w/L = 2/1$ ,  $V_{TO} = 1V$ ,  $k_P = 50$ .  
 PMOS =  $w/L = 4/1$ ,  $V_{TO} = -1V$ ,  $k_P = 25$   
 $V_{DD} = 5V$



- a)  $V_{in} = 0V$  determine  $V_{out}$  so NMOS and PMOS currents are equal.  
 Explain.

A: If  $V_{in} = 0V$  then NMOS is off, making NMOS current  $\emptyset$ . For PMOS current to be  $\emptyset$ ,  $V_{DD}$  and  $V_{out}$  must be equal.

So  $V_{out} = V_{DD} = 5V$

PMOS and NMOS current =  $\emptyset$

- b)  $V_{in} = 5V$ , determine  $V_{out}$  so that NMOS and PMOS current are equal

PMOS is off so current  $\emptyset$

NMOS current is  $\emptyset$  only when  $V_{out} = 0V$

- c) Calculate on-resistance of NMOS when  $V_{in} = V_{DD}$

$$R_{on} = \frac{1}{k_P \cdot \frac{w}{L} (V_{in} - V_{TO})} = \boxed{2.5 \text{ k}\Omega}$$

- 11) a) Out of the intrinsic  $C_{GS}$ ,  $C_{GD}$ , which is larger when  $V_{GS} = V_{DS} = V_{DD}$ ? Is the transistor in saturation or linear?

A: When  $V_{GS} = V_{DS} = V_{DD}$  the transistor is in saturation

In saturation:  $C_{GS} = \frac{3}{2} C_{GC}$  and  $C_{GD} = 0$  so  $C_{GS} > C_{GD}$

- b) Out of the extrinsic  $C_{GS}$ ,  $C_{GD}$ , and  $C_{GB}$ , which ones are proportional to channel width? And which to length?


$C_{GS}$  and  $C_{GD}$  are  $W$

$C_{GB}$  is  $L$

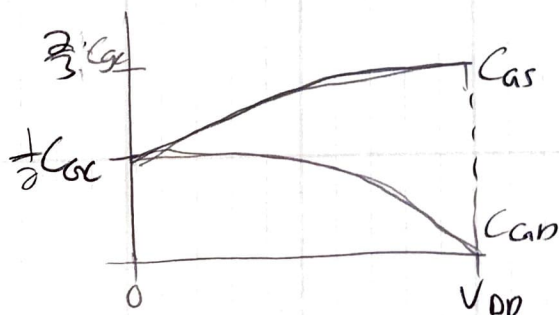- c) How do the transistor intrinsic channel  $C_{GS}$  and  $C_{GD}$  vary with increasing  $V_{DS}$  from 0V to  $V_{DD}$ ?

Assume  $V_{GS}$  is well above threshold. Sketch the

curves. At what biasing condition is  $C_{GS} = \frac{1}{2} C_{GS}'' WL$ ?



Farrad bias mode yields

$$C_{GS} = \frac{1}{2} C_{GS}'' WL \text{ when } V_{DS} = 0V$$