

ELEC 2210 Fall 2020

Lab 4 Quiz

Name: Jacob Howard

Section: 002 (Tues 1:00pm)

1. What is the difference between a half-adder and a full-adder?

A. Carry out

B. **Carry in** (Full adder has carry in)

C. Carry out and Carry in

D. Sum

2. Convert the decimal number 50 into binary and hexadecimal.

Dec to Bin = 110010


Dec to Hex = 32

3. What is the sum of binary numbers 110010 and 101111?

Binary = 110001

Dec = 97

Prelab Screenshots

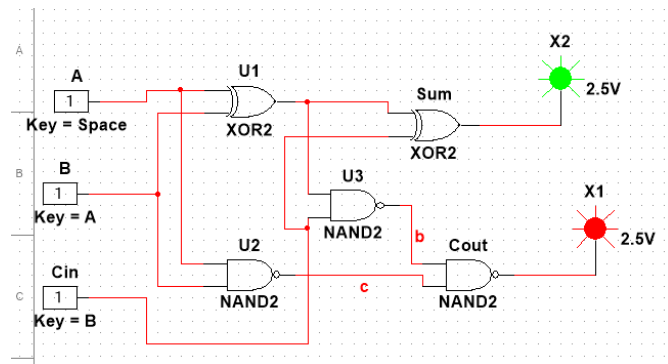

Inputs			Base 10 Sum of $A+B+C_{IN}$	Binary Outputs	
A	B	C_{IN}		C_{OUT}	S
0	0	0	0	0	0
0	0	1	1	0	1
0	1	0	1	0	1
0	1	1	2	1	0
1	0	0	1	0	1
1	0	1	2	1	0
1	1	0	2	1	0
1	1	1	3	1	1

C
C
C
C
C
C
C
C

C is for correct. The truth table checks out

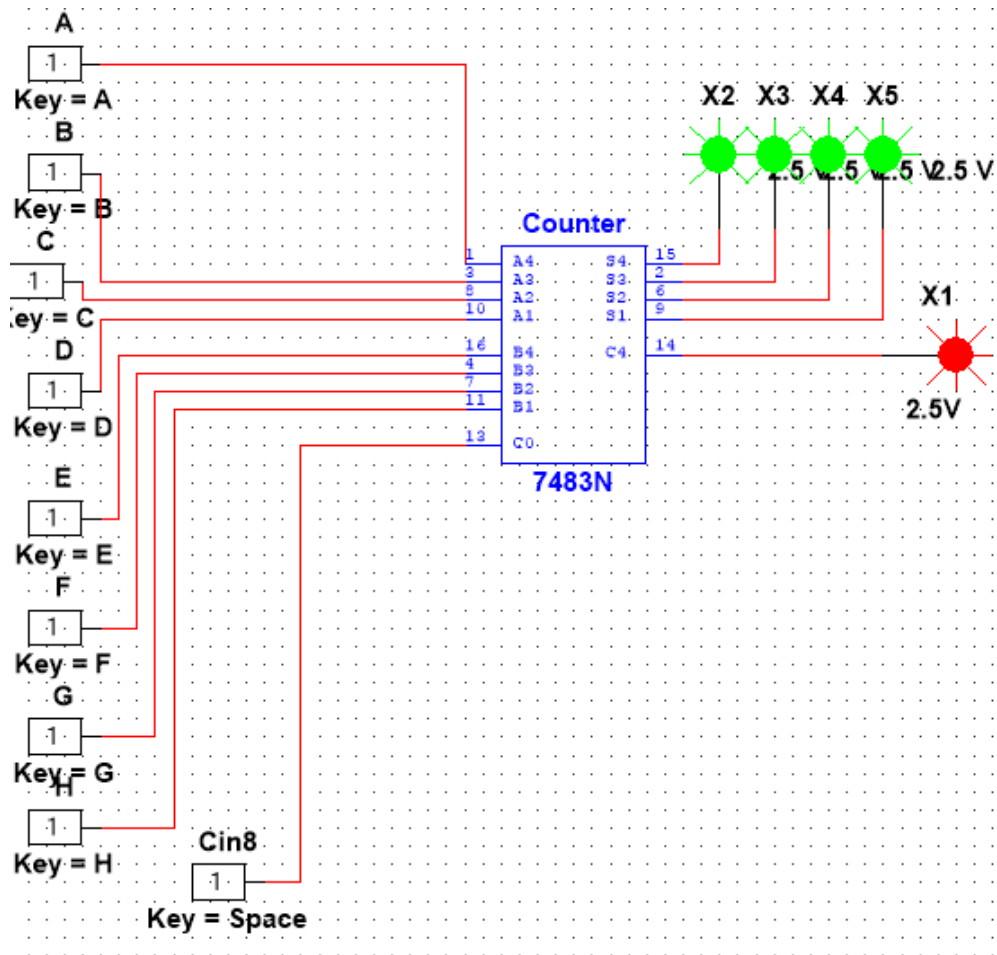


Table 6. Test results for the 4-bit full adder circuit. All values in hex.

Inputs			Calculated Outputs		Actual Outputs		Check here if correct.
A	B	C _{IN}	C _{OUT}	S	C _{OUT}	S	
0	0	0	0	0	0	0	
0	0	1	0	1	0	1	
1	0	0	0	1	0	1	
7	7	1	0	F	0	F	
8	7	0	0	F	0	F	
8	8	0	1	0	1	0	
F	F	0	1	F	1	F	
F	F	1	1	F	1	F	