

ELEC-5200

Computer Architecture

FROM: Jacob Howard


TO: Dr. Harris & Tucker Johnston

DUE DATE: 10/27/21

CPU Design – Part 3

Datapath

This is an overview of the Datapath design I created in Part 2. I noticed one flaw in the design where the ALU Control was connected to the RegisterFile/SignExtended MUX instead of to the ALU. The correction is drawn in highlighted pen to show the flaw and correction. I will officially fix this problem on the datapath design. Use this datapath as a reference to why designs were made in the Verilog Design.

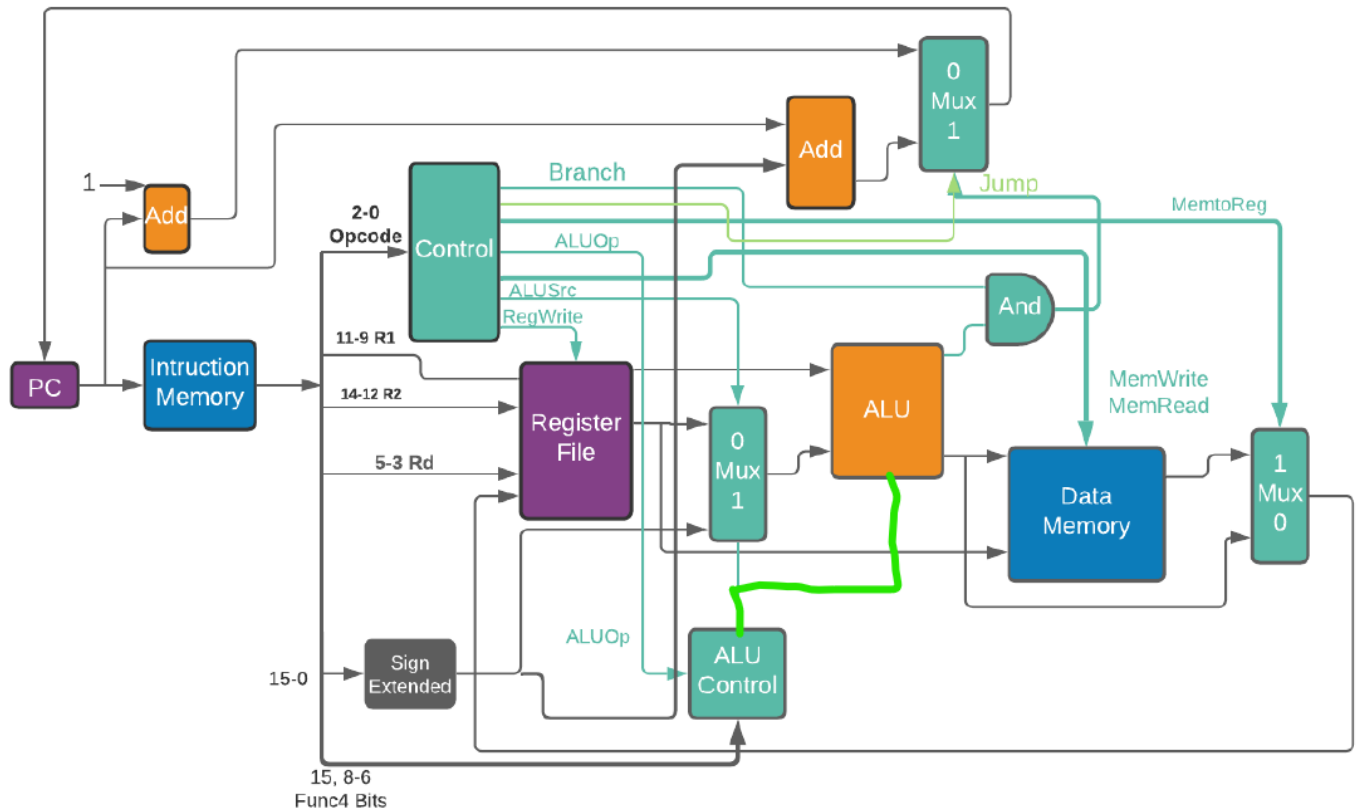


Verilog Design

I will go over my design for each major component in my datapath. All full Verilog code will be shown at the bottom of this report, while I will show parts of my design here to describe design decisions and any simulations that may be useful.

PC

 The PC was the first major component I design in Verilog and is the component that points to which instruction will be called next from the instruction memory. The PC is the only thing affected by clock and reset inputs. A simulation of the PC counting up 1 based off of the MUX output and being reset back to zero is shown below. The code can be found at the bottom of the report.




Instruction Memory

Next I implemented the instruction memory component. This component will store all instructions in a ROM file and read lines based on where the PC tells it to. It will output a 16-bit word instruction for all other components to use. The code is shown at the bottom of the report and is labeled.

Control Unit

Next I created the control unit, which decodes the opcode. When decoded, different signals are sent out based on the type of instruction. The control unit determines whether the instruction is R-Type, I-Type, S-Type, SB-Type, or UJ-Type and sends signals to other components based on the decoded type. We can see in the simulation below that based on the opcode, the correct signals are sent out to the other components. The Control Unit code can be seen at the bottom of this report labeled.

 

Sign Extended

For the Sign Extended block, I made some engineering decisions that should help my immediate values be correct regardless of type. I chose to decode the type in the sign extended block and based off the type, I would parse the immediate values accordingly and send the parsed immediate value to the output. Shown below is a snippet of code for parsing an SB-Type Instruction and sending the correct immediate value to the ALU/Adder2. From the table shown below, you can see why it is important to parse the values correctly based on each type. In our simulation, we can see that the sign extended block correctly parses sb-type instructions. The simulation is shown below.

```
sbType: begin //SB-Type instructions
    parseSB[3] = InstructionMemory[15];
    parseSB[2:0] = InstructionMemory[5:3];
    signIout[3:0] = parseSB[3:0]; //output
```

Type	15 th bit	14-12	11-9	8-6	5-3	2-0 bits
R-Type	Func4[3]	R2	R1	Func4[2:0]	Rd	opcode
I-Type	Imm[3:0]		R1	Func4[2:0]	rd	opcode
S-Type	Imm[3]	R2	R1	Func4[2:0]	Imm[2:0]	opcode
SB-Type	Imm[3]	R2	R1	Func4[2:0]	Imm[2:0]	opcode
UJ-Type	Imm[9:0]				rd	opcode



Register File

Next, I designed the register file. I designed the Register File to have 8 registers, as that is all that my 16-bit word instructions will allow. I made inputs for reading address 1&2 and writing data correctly to the register file. I will show my code directly below as it is not too long and will explain how I designed all 8 registers.

```
//inputs/outputs above this
reg [15:0] REG_FILE [0:7];

assign RegReadData1 = REG_FILE[RegReadAddr1];
assign RegReadData2 = REG_FILE[RegReadAddr2];

initial begin
    REG_FILE[0] = 0;
    REG_FILE[1] = 0;
    REG_FILE[2] = 0;
    REG_FILE[3] = 0;
    REG_FILE[4] = 0;
    REG_FILE[5] = 0;
    REG_FILE[6] = 0;
    REG_FILE[7] = 0;
```

```

end


always @ (*) begin
    if (RegWrite) //if RegWrite is enabled
        REG_FILE[RegWriteAddr] = RegWriteData;
        REG_FILE[0] = 0;
    end
endmodule

```

ALU Control

Before I talk about the ALU, I need to discuss my design for the ALU Control Unit and how it works. I designed my ALU Control to decode my Function Bits based off the type. Since my function bits are only 4-bits long and other types share the same function bits, I had to first decode the type of instruction. Once the type was determined, I could then decode the exact instruction to be performed. The way I did this was have my Opcode Control Unit send a number (0-7) to the ALU Control to determine the type. For example, an ALUOp signal of zero would be arithmetic type, while a signal of 1 would be immediate arithmetic, and so on. Once the type was determined, I looked at the function bits to decode the exact instruction to send to the ALU. The ALU will get a signal of 1-20 based on the exact instruction it should perform. 1 would be an ADD instruction where as 20 would be the JALR instruction.

 We can see from the simulation below, when testing for an ADD instruction, we get an output of 1, and when testing for an ADDI instruction we get an output of 8 as expected. This is how the ALU will know what operation to perform. The code can be seen at the bottom of the report, labeled.



ALU


Lastly, I designed the ALU. The ALU takes the output from the ALU control to determine the instruction to do. Once the instruction is determined it will take register values and perform operations. A code snippet of instruction values are shown below and the entire code can be seen at the bottom of the report. When testing the ADDi instruction in simulation (making sure the ALUControl signal is 1 for ADD), we see that $r1+r2$ is performed and stored into rd. The simulation can be seen below.

```

//Arithmetic
ADD = 1,
SUB = 2,
AND = 3,
OR = 4,
XOR = 5,
SL = 6,

```
 
```
SR = 7,  
  
//Immediate Arithmetic  
ADDI = 8,  
ANDI = 9,  
ORI = 10,  
XORI = 11,  
SLI = 12,  
SRI = 13,  
//load/store instructions  
LOAD = 14,  
STORE = 15,  
//Branch Instructions  
BEQ = 16,  
BGT = 17,  
BGE = 18,  
BLT = 19,  
//JALR Instruction  
JALR = 20;
```



All Other Components

The Data Memory was not required to be completed in this part, so it is not finished for this design. The PC+1 adder and PC+SignExtended adder are not shown along with the MUX's and AND Gate as these are not “Main” components. They are designed in Verilog, but are not required to show in this report and their functionality is easy to understand based off looking at the DataPath.

All Verilog Code

PC

```
module PC(  
    input clk, //the clock  
    input reset, //resets PC  
    input [9:0] MUX2, //the input from MUX2 will change the count on PC  
    output reg PC //the output of pc will tell instuction memory where to point  
);  
  
begin  
    always @(clk | reset)  
  
        if (reset == 1) begin //if reset is active, reset pc to 0  
            PC = 0; //resets PC to 0  
        end  
  
        else begin //if reset is not active, then PC will equal MUX2  
            PC = MUX2; //mux2 is the PC mux. It will either equad PC+1 or PC +branch/jump location  
        end  
end  
endmodule
```

Intruccion Memory

```
module IntructionMemory(  
    input [15:0] Addr,  
    input [15:0] data  
);  
  
reg [15:0] ROM [0:65535];  
  
initial $readmemb("intruction_mem.mem", ROM);  
  
assign data = ROM[Addr];  
  
endmodule
```

Control Unit

```
module ControlUnit(  
    input [2:0] opcode,  
    output reg branch,  
    output reg jump,  
    output reg mem_read_write,  
    output reg mem_to_reg,  
    output reg ALUOp,
```

```
output reg ALUSrc,
output reg RegWrite,
output reg halt
);
//Opcode of all instructions
parameter ALU_A = 3'b000,
          ALU_I = 3'b001,
          LOAD = 3'b010,
          STORE = 3'b011,
          BRANCH = 3'b100,
          JAL = 3'b101,
          JALR = 3'b110,
          HALT = 3'b111;

always @ (opcode) //opcode change
begin
branch = 0;
jump = 0;
mem_read_write = 0; //do nothing
ALUOp = 0;
ALUSrc = 0;
RegWrite = 0;
halt = 0;

case (opcode)

  ALU_A: begin //Arithmetic Instructions
    ALUOp = 0; //operation 0, Arithmetic instructions
    ALUSrc = 0;
    RegWrite = 0; //sets zero on mux1 (register/sign mux)
    mem_to_reg = 0;
  end

  ALU_I: begin //Immediate Instructions
    ALUOp = 1; //operation 1, immediate arithmetic
    ALUSrc = 1; //gets immediate sign extended from mux
    RegWrite = 1;
    mem_to_reg = 0;
  end

  LOAD: begin //Load Word Instruction
    ALUOp = 3; //operation 3, load word
    ALUSrc = 1; //for immediates
    mem_read_write = 1; //read memory
    RegWrite = 1;
    mem_to_reg = 1; //memory
  end
```



```

STORE: begin //Store Word Instruction
ALUOp = 5; //operation 5, store word
ALUSrc = 1;
mem_read_write = 2; //write memory (2 because we want zero to not read nor write to memory)
end

BRANCH: begin //branch instructions
branch = 1;
ALUOp = 6; //operation 6, branch
ALUSrc = 1;
end

JAL: begin //Jump and Link Intruction
jump = 1;
RegWrite = 1;
mem_read_write = 2;
end

JALR: //Jump and Link Register Intruction
begin
ALUOp = 7; //operation 7, jump and link register (regular jump does not require operation)
ALUSrc = 1; //Immediate
RegWrite = 1;
mem_read_write = 2;
end

HALT: begin
halt = 1; //halts everything :)
end

endcase

end

endmodule

```

Sign Extended Unit

```

module SignExtended(
input [15:0] InstructionMemory,
output reg [9:0] signlout //sign extended immediates output. Max value should not be over 10-bits
);
//parsing data for immidiates values
reg [3:0] parsel;
reg [3:0] parseSB;
reg [9:0] parseUJ;
reg [3:0] parseLW;
reg [3:0] parseSW;

```

```
//opcode
reg [2:0] opcode;

//parameters used to know how to parse immediate output
parameter iType = 3'b001,
          sbType = 3'b100,
          ujType = 3'b101,
          lw = 3'b010,
          sw = 3'b011;

always @ (InstructionMemory)
begin
//clears everything to zero
signlout = 0; //setting output to zero
opcode = 0;
parseI = 0;
parseSB = 0;
parseUJ = 0;
parseLW = 0;
parseSW = 0;
//setting opcode
opcode[2:0] = InstructionMemory[2:0]; //assigning opcode as first 3-bits from memory instructions
case (opcode)

    iType: begin //I-Type instructions
        parseI[3:0] = InstructionMemory[15:12];
        signlout[3:0] = parseI[3:0]; //sets output to the parsed immediates
    end

    sbType: begin //SB-Type instructions
        parseSB[3] = InstructionMemory[15];
        parseSB[2:0] = InstructionMemory[5:3];
        signlout[3:0] = parseSB[3:0];
    end

    ujType: begin //UJ-Type instruction
        parseUJ[9:0] = InstructionMemory[15:6];
        signlout[9:0] = parseUJ[9:0];
    end

    lw: begin //load word is i-type parsing
        parseLW[3:0] = InstructionMemory[15:12];
        signlout[3:0] = parseLW[3:0];
    end

    sw: begin //store word is s-type parsing and same as sb-type parsing
        parseSW[3] = InstructionMemory[15];
```

```
    parseSW[2:0] = InstructionMemory[5:3];
    signlout[3:0] = parseSW[3:0];
end
endcase

end
endmodule
```

ALU Control

```
module ALUControl( //tells ALU what operation to perform
input ALUOp,
input [8:6] InstructionMemory,
output reg [4:0] control
);

parameter //Arithmetic
    A = 0, //Arithmetic instructions
    ADD = 4'b0000,
    SUB = 4'b0001,
    AND = 4'b0010,
    OR = 4'b0011,
    XOR = 4'b0100,
    SL = 4'b0101,
    SR = 4'b0110,
    //Immediat Arithmetic
    I = 1,
    ADDI = 4'b0000,
    ANDI = 4'b0001,
    ORI = 4'b0010,
    XORI = 4'b0011,
    SLI = 4'b0100,
    SRI = 4'b0101,
    //Load Instruction
    LOAD = 3, //only 1 instruction
    //Store Instruction
    STORE = 4, //only 1 instruction
    //Branch
    BRANCH = 6,
    BEQ = 4'b0000,
    BGT = 4'b0001,
    BGE = 4'b0010,
    BLT = 4'b0011,
    //Jump and Link Reg
    JALR = 7; //only 1 instruction

always @ (ALUOp)
begin
```

```
control = 0; //sets control to zero at start so no instructions are performed
case (ALUOp)

  A: begin //arithmetic
    case (InstructionMemory) //Intruction decoder
      ADD: begin
        control = 1;
      end
      SUB: begin
        control = 2;
      end
      AND: begin
        control = 3;
      end
      OR: begin
        control = 4;
      end
      XOR: begin
        control = 5;
      end
      SL: begin
        control = 6;
      end
      SR: begin
        control = 7;
      end
    endcase //end instruction decoder case
  end

  I: begin //Immediate math
    case (InstructionMemory) //Intruction decoder
      ADDI: begin
        control = 8;
      end
      ANDI: begin
        control = 9;
      end
      ORI: begin
        control = 10;
      end
      XORI: begin
        control = 11;
      end
      SLI: begin
        control = 12;
      end
      SRI: begin
        control = 13;
```

```
        end
    endcase //end instruction decoder case
end

LOAD: begin //Load Word
    control = 14;
end
STORE: begin //Load Word
    control = 15;
end

BRANCH: begin //Branch Instructions
    case(InstructionMemory) //decoder case
        BEQ: begin
            control = 16;
        end
        BGT: begin
            control = 17;
        end
        BGE: begin
            control = 18;
        end
        BLT: begin
            control = 19;
        end
    endcase//end instruction decoder case
end

JALR: begin
    control = 20;
end

endcase //endcase for ALUOperation case

end

endmodule
```

ALU

```
module ALU (
    //temp input/output of reg for testing
    input [1:0] r1,
    input [1:0] r2,
    output reg [3:0] rd,

    input regFile,
    input mux2, //mux for regFile/SignExtended
```

```
input ALUControl,
output reg data,
output reg branch_gate //compare output for branches
);

//wire r1;
//wire r2;
wire i = mux2; //immediate (sign extended will handle immediate field from opcode)
//reg rd;

parameter //Arithmetic
    ADD = 1,
    SUB = 2,
    AND = 3,
    OR = 4,
    XOR = 5,
    SL = 6,
    SR = 7,
    //Immediate Arithmetic
    ADDI = 8,
    ANDI = 9,
    ORI = 10,
    XORI = 11,
    SLI = 12,
    SRI = 13,
    //load/store instructions
    LOAD = 14,
    STORE = 15,
    //Branch Instructions
    BEQ = 16,
    BGT = 17,
    BGE = 18,
    BLT = 19,
    //JALR Instruction
    JALR = 20;

always @(ALUControl) //ALUControl will output a number from 0-20 so the ALU will know what operations to
perform
begin
    //setting ALU outputs to 0 at the beginning
    data = 0;
    branch_gate = 0;

    case (ALUControl)
        //Arithmetic
        ADD: begin
            rd = r1+r2;
```

```
end
SUB: begin
rd = r1-r2;
end
AND: begin
rd = r1&r2;
end
OR: begin
rd = r1 | r2;
end
XOR: begin
rd = r1^r2;
end
SL: begin
rd = 1<<r1;
end
SR: begin
rd = 1>>r1;
end
//Immediate Arithmetic
ADDI: begin
rd = r1+i;
end
ANDI: begin
rd = r1&i;
end
ORI: begin
rd = r1 | i;
end
XORI: begin
rd = r1^i;
end
SLI: begin
rd = 1<<i;
end
SRI: begin
rd = 1>>i;
end
//Load/Store Word
LOAD: begin
rd = r1+i;
end
STORE: begin
//finish later
end
//Branch
BEQ: begin
  if (r1 == r2) begin
```

```
    branch_gate = 1; //allowing a branch because terms are met
  end
  else begin
    branch_gate = 0; //terms not met, not allowing branch
  end
end
BGT: begin
  if (r1 > r2) begin
    branch_gate = 1; //allowing a branch because terms are met
  end
  else begin
    branch_gate = 0; //terms not met, not allowing branch
  end
end
BGE: begin
  if (r1 >= r2) begin
    branch_gate = 1; //allowing a branch because terms are met
  end
  else begin
    branch_gate = 0; //terms not met, not allowing branch
  end
end
BLT: begin
  if (r1 > r2) begin
    branch_gate = 1; //allowing a branch because terms are met
  end
  else begin
    branch_gate = 0; //terms not met, not allowing branch
  end
end
//Jump and Link Register
JALR: begin
  //finish
end
endcase

end
endmodule
```