

ELEC-4200

Digital System Design

FROM: Jacob Howard

TO: Prof. Ujjwal Guin

DUE DATE: 4/8/21


Lab 9

Introduction

The goal of this lab was to familiarize ourselves with Algorithmic State Machines (ASM). We were required to learn and use ASM chart techniques for development in this lab.

Task 1

In Task 1, we were asked to design a 3-Bit x 3-Bit binary multiplier. The design was a bit more complicated when we were told we had to use a 3-bit accumulator, a 3-bit multiplier register, a 3-bit adder, a counter, and a 3-bit shifter. Instead of having Verilog do all the hard work of multiplication while we would just code, for example, $a * b = \text{output}$, we were designed a multiplier ourselves with logic design. We did this using ASM and coding a finite state machine. The code can be seen below in Code 1. We were also asked to create a test bench and simulate the code. The testbench can be seen in Testbench 1 and the simulation in Simulation 1 below.

 

Simulation 1

```
module Task1_new (multiplicand, multiplier, clk, start,
product, done);
input [2:0] multiplicand;
input [2:0] multiplier;
input clk, start;
output reg [5:0] product;
output reg done;
reg [6:0] acc;
integer n = 0;
reg [6:0] Q;
reg [1:0] state, nextstate;
parameter [1:0] S0=0, S1=1, S2=2;
//Main Code
////////////////////////////////////
always @ (posedge clk)
state <= nextstate;

//begin
always @(state or posedge start)
begin
    nextstate = 1'b0;
//    done = 0;
    case(state)
    //Start State
    S0: if (start)
        begin
            acc[6:3] = 4'b0000;
            acc[2:0] = multiplier;
            done = 0;
            n = 0;
            nextstate = S1;
        end
    //if start 0
    else
        nextstate = S0;
    //accumulate state
    S1: if (acc[0] == 1 & n <= 2)
        begin
            acc[6:3] = acc [6:3] + multiplicand;
            nextstate = S2;
        end
    else
        nextstate = S2;
    //shift state
    S2: if (n <= 2)
        begin
            acc = {1'b0, acc[6:1]};
            product = acc[5:0];
            n = n + 1;
            nextstate = S1;
        end
    else
        begin
            done = 1;
            nextstate = S0;
        end
    end
end
```

```
    endcase  
end  
endmodule
```

Code 1

```
module Task1_tb();  
reg [2:0] multiplicand;  
reg [2:0] multiplier;  
reg clk, start;  
wire [5:0] product;  
wire done;  
  
integer k;  
  
Task1_new MUL (.multiplicand(multiplicand),  
.multiplier(multiplier),  
.clk(clk), .start(start), .product(product), .done(done));  
  
initial begin  
#500 $finish; //runs simulation 100 times  
end  
  
//clock  
    initial begin  
        clk = 0;  
        for (k = 0; k <= 1000; k = k+1)  
            begin  
                #5 clk = 1;  
                #5 clk = 0;  
            end  
    end  
  
//start  
    initial begin  
        start = 0;  
        #30 start = 1;  
        #10 start = 0;  
        #100 start = 1;  
        #10 start = 0;  
        #100 start = 1;  
        #10 start = 0;  
    end  
  
    initial begin  
        multiplicand = 3'b111;  
        multiplier = 3'b101;  
        #140  
        multiplicand = 3'b100;  
        multiplier = 3'b001;  
        #110  
        multiplicand = 3'b111;  
        multiplier = 3'b100;  
    end  
endmodule
```

Testbench 1

Task 2

In Task 2, all we were asked to do was physically test the design on the board. We were asked to assign switches 5-7 as the multiplier input, switches 2-4 as the multiplicand input, switch 15 as the clock input, and button U as the start input. My design worked as intended when testing on the board and was verified by the TA.

Task 3

In Task 3, we were asked to modify the design of task 1 to perform a 4-bit by 4-bit unsigned multiplication. We were told to store the multiplicand and multiplier input values in a 32x4 ROM file. We were also asked to use the onboard clock at 100 Mhz as the clock and have the output displayed on 7-segment displays. Sadly, due to errors in my Task 1 code through the lab, I was unable to get to Task 3 to design and implement the task. I later fixed Task 1 with help of the TA but was never able to design and test Task 3.

Conclusion

In conclusion, this lab was more difficult than it first seemed. I had trouble implementing the multiplier with the desired specifications at first. I had multiple solutions that physically worked, but would not give me the correct simulation results. I fully designed a code that worked on the board and displayed the correct simulation with the help of the TA. Overall, this lab was more challenging than I first assumed but was able to figure out most of the lab by the end of lab time.